

**Jim Siegrist**  
**Phone: 486-4397**  
**Email: [JLSiegrist@lbl.gov](mailto:JLSiegrist@lbl.gov)**  
**Room (at LBL): 50-4055**


**Advice:**

Today: lec 9 OP AMP III  
 lec 10 TH Mar 15  
 lec 11 TH Mar 22  
 lec 12 TUE Apr 3 Last Lecture!!


Final project proposals (< ½ page) due Monday, March 19. I sign off, talk to TA's first.  
 Problems 8.12, 8.13 → supplementary.

**Circuit Analyses**

Frequency Response, General Circuit

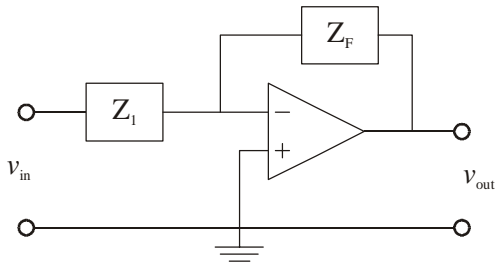

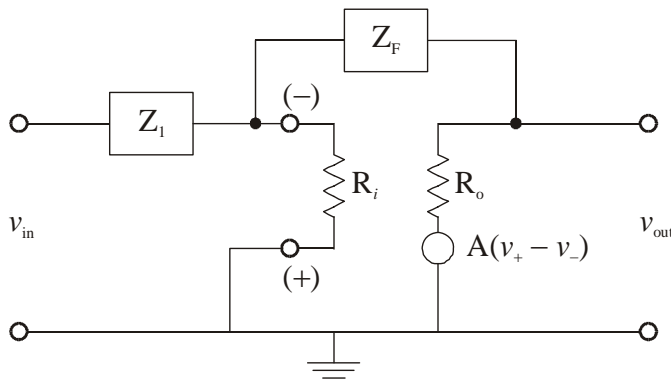Substitute the op-amp model: ( $A = A(\omega) \rightarrow$  small at large  $\omega$ )



Node equations at  $v_-$  and  $v_{out}$ :

$$(1) \frac{v_- - v_{in}}{Z_1} + \frac{v_- - v_{out}}{Z_F} + \frac{v_-}{R_i} = 0$$

$$(2) \frac{v_{out} - v_-}{Z_F} + \frac{v_{out} - A(0 - v_-)}{R_o} = 0$$

$$A' = \frac{v_{out}}{v_{in}}$$

Solve (2) for  $v_-$  in terms of  $v_{out} \Rightarrow$

$$v_{out} \left( \frac{1}{Z_F} + \frac{1}{R_o} \right) + v_- \left( \frac{A}{R_o} - \frac{1}{Z_F} \right) = 0$$

$$\Rightarrow v_- = \frac{v_{out}}{(Z_F \parallel R_o) \left( \frac{1}{Z_F} - \frac{A}{R_o} \right)}$$

From (1),

$$v_- \left( \frac{1}{Z_1} + \frac{1}{Z_F} + \frac{1}{R_i} \right) - \frac{v_{out}}{Z_F} = \frac{v_{in}}{Z_1}$$

$$\Rightarrow v_{out} \left[ \left( \frac{1}{Z_1} + \frac{1}{Z_F} + \frac{1}{R_i} \right) \frac{1}{(Z_F \parallel R_o) \left( \frac{1}{Z_F} - \frac{A}{R_o} \right)} - \frac{1}{Z_F} \right] = \frac{v_{in}}{Z_1}$$

$$\Rightarrow A' = \frac{v_{out}}{v_{in}} = -\frac{Z_F}{Z_1} \left[ \frac{1}{1 - \left( \frac{1}{Z_1} + \frac{1}{Z_F} + \frac{1}{R_i} \right) \left( \frac{1}{Z_F} + \frac{1}{R_o} \right) \frac{Z_F}{\left( \frac{1}{Z_F} - \frac{A}{R_o} \right)}} \right]$$

$$= -\frac{Z_F}{Z_1} \left[ \frac{1}{1 - \left( \frac{1}{Z_1} + \frac{1}{Z_F} + \frac{1}{R_i} \right) (R_o Z_F + Z_F^2) \frac{1}{(R_o - A Z_F)}} \right]$$

$\lim R_o \rightarrow 0, R_i \rightarrow \infty \rightarrow$

$$= -\frac{Z_F}{Z_1} \left[ \frac{1}{1 + \left( \frac{1}{Z_1} + \frac{1}{Z_F} \right) \frac{Z_F}{A}} \right] = -\frac{Z_F}{Z_1} \left[ \frac{A}{A + 1 + \frac{Z_F}{Z_1}} \right]$$

As gain gets small,

$$A' \sim -\frac{Z_F A}{Z_1} \frac{Z_1}{Z_F + Z_1}$$

$$\sim \frac{-AZ_F}{Z_F + Z_1} \rightarrow 0$$

Also, just rearranging terms,

$$A' = \frac{A \left( -\frac{Z_F}{Z_1} \right) \left( \frac{Z_1}{Z_1 + Z_F} \right)}{A + \left( \frac{Z_1 + Z_F}{Z_1} \right) \left( \frac{Z_1}{Z_1 + Z_F} \right)} = \frac{A \left( \frac{-Z_F}{Z_1 + Z_F} \right)}{1 + A \left( \frac{Z_1}{Z_1 + Z_F} \right)}$$

### Stability

Instability most often occurs when output appears for no input → oscillations.  
Signal suffers a phase shift passing through amp.

Typically,

- ~ 0 at low frequency
- increases at higher frequencies
- -1 at 180° ⇒
- negative feedback at low  $\nu$  becomes positive at high  $\nu$

General form for gain ~

$$A' = \frac{c(\omega)A(\omega)}{1 + A(\omega)f(\omega)}$$

$c(\omega)$  depends on form of circuit

$f(\omega)$  is called feedback coefficient

if  $A(\omega)f(\omega) = -1$  (for some  $\omega$ ), instability results

Turns out, if  $|Af| \geq 1$  for  $\omega$  whose phase shift is  $-180^\circ$ , instability occurs (Nyquist Criterion)


For voltage follower, (last time)

$$A' = \frac{A}{1 + A} \Rightarrow c = f = 1$$

$$\& \Rightarrow c = \frac{-Z_F}{Z_1 + Z_F}$$


$$f = \frac{Z_1}{Z_1 + Z_F} \quad \text{for inverter (see previous pg)}$$

Suppose: (follower)

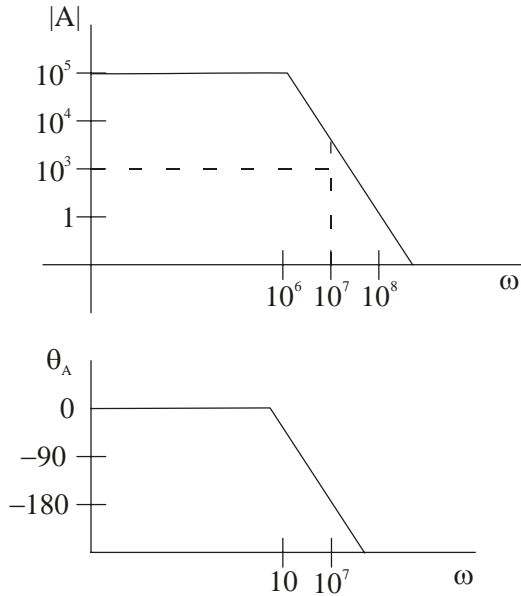

$-180^\circ \Rightarrow \omega \sim 10^7$   
 $A = \text{gain} \sim 10^4 \text{ at } 10^7 \Rightarrow |Af| \gg 1 \Rightarrow \text{oscillations}$

Op-Amp design:

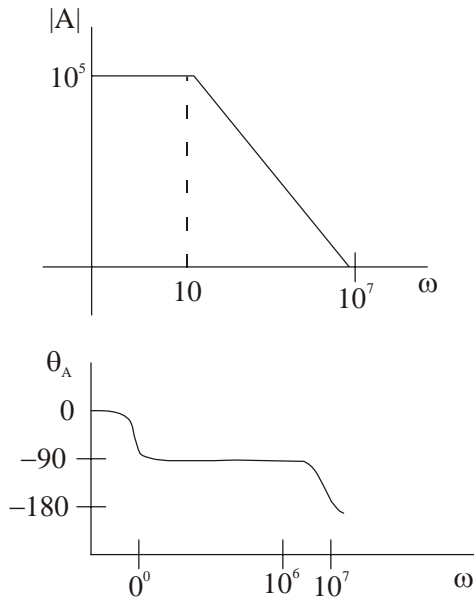

$\omega \sim 10^7, |A| \sim +10^{-1} \Rightarrow \text{stable}$   
 Obtain by putting RC filter someplace in op-amp  
 (rolloff at  $|A|$  20db/decade, phase shift of  $90^\circ$ )  
 More phase shifts from stray capacitance at higher  $\nu$ , but  $|A|$  already  $< 1$   
 emphasize  $\Rightarrow$  why leads must be short, circuits neat


Summary of Op-Amp

- Op amps are cheap, versatile, and form building blocks for circuits  
 $A = \infty$
- Ideal op-amp:  $R_i = \infty$   
 $R_o = 0$
- Offsets
- MSR
- Negative feedback provides de-sensitivity of op-amp characteristics
- Limited frequency response – pass band with negative feedback much larger
- Improper feedback  $\Rightarrow$  oscillations

**Instruments & Devices**


Transistors

Transistors are control elements

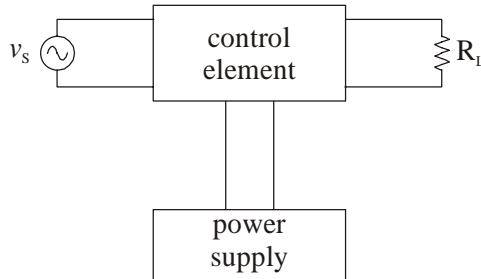

Take a small input signal & amplify it, with the power to do so coming from the external DC sources.

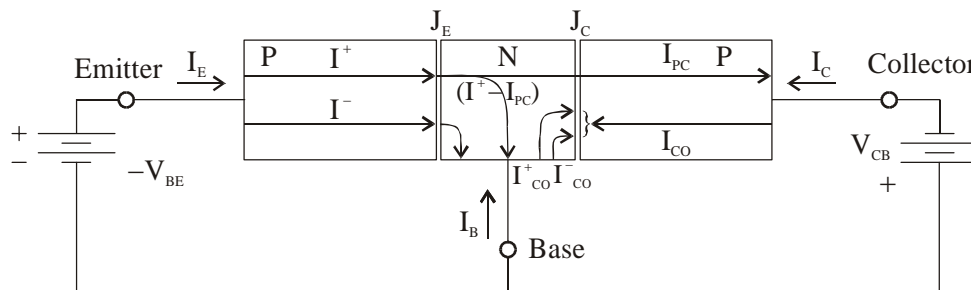Bipolar: current-operated, 3-terminal device consisting of one forward & one reverse biased diode, with base region in common



Emitter-Base is forward biased by  $(-)V_{BE} \Rightarrow$

Majority carriers (hole) are injected into base where they drift to collector.  $(I^+)$  (diffusion gradient)

Electron current  $(I^-)$  from base to emitter is made small by construction (doping – emitter much more heavily doped)

Total emitter current =  $I_E = I^+ + I^-$

Some holes reach collector, rest are recombined in the base.

$I^+ - I_{pc}$  go out through base

$I_{pc}$  go to collector

Reverse current  $I_{co}$  from collector to base

$I_{co}^+$  = holes moving from N to P across  $J_c$

$I_{co}^-$  = electrons moving from P to N across  $J_c$

$-I_{co} = I_{co}^+ + I_{co}^-$  – sign convention so  $I_{co}$  in direction  $I_c$

Holes generated thermally within the base

Total collector current:

$$I_c = I_{co} - I_{pc} \equiv I_{co} - \alpha I_E$$

or

$$\alpha \equiv -\frac{I_c - I_{co}}{I_E} \quad \text{large-signal current gain}$$


$\alpha$  always  $> 0$ , ranges from .90 – .998, varies with  $I_E$ ,  $V_{CB}$ , temperature

Also,  $\beta \equiv \frac{\alpha}{1 - \alpha}$ ; in CE configuration,


$$I_c \sim \beta I_{base}$$

$\Rightarrow \beta$  is current gain of the device; current operated device!!

Circuit Symbols:

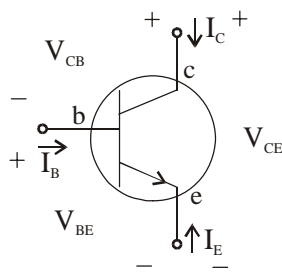

N-P-N

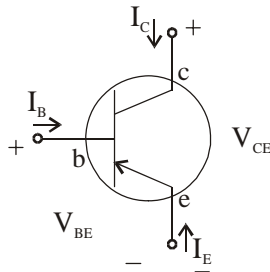

P-N-P


Identical, arrow opp.

[Current in emitter is positive in the direction of the arrow on the emitter lead]

3 terminals  $\Rightarrow$  6 ways to connect

Closing Comments:

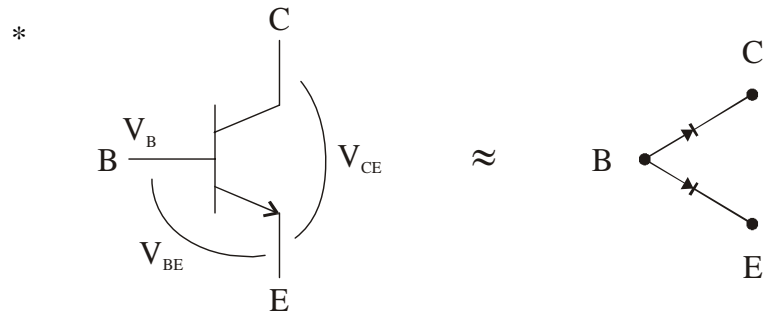\*  $V_{CE} > 0$ , collector more positive than emitter



\* limits on  $I_C$ ,  $I_B$ ,  $V_{CE}$  max power dissipation, etc.

$$P_{\max} = (I_C V_{CE})_{\max}$$

\*  $V_B \sim V_E + .6$  in active gain region (when ‘on’)  
 $= V_E + V_{BE}$

\*  $I_C \approx \beta I_B$

current operated device

detailed use of this in lecture 11 – push-pull case